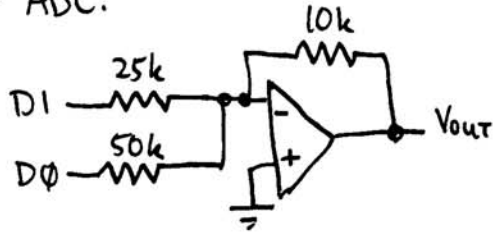


Digital to Analog Conversion


Example of 2-bit ADC:

D1	D0	Vout
0	0	0
0	1	1V
1	0	2V
1	1	3V

1 ↔ 5V



Flash ADC

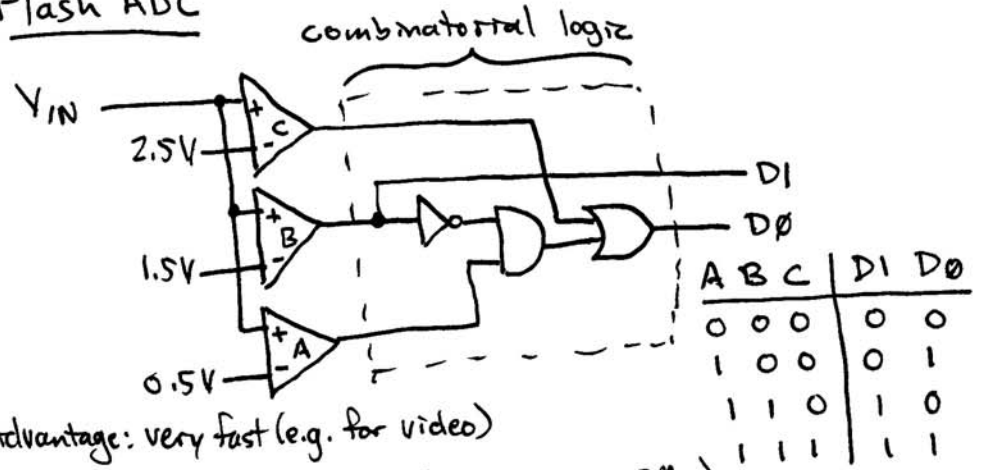

Advantage: very fast (e.g. for video)

Disadvantage: lots of hardware (# of comparators =  $2^n - 1$ )

A	B	C	D1	D0
0	0	0	0	0
1	0	0	0	1
1	1	0	1	0
1	1	1	1	1

Analog to Digital Conversion


Example: 2-bit ADC:

Vin	D1	D0
-0.5 to 0.5V	0	0
0.5 to 1.5V	0	1
1.5 to 2.5V	1	0
2.5 to 3.5V	1	1

Resolution =  $\frac{\text{range}}{2^n}$  ← # of bits

Conversion time = time between when we ask the ADC to do a conversion & when it finishes.

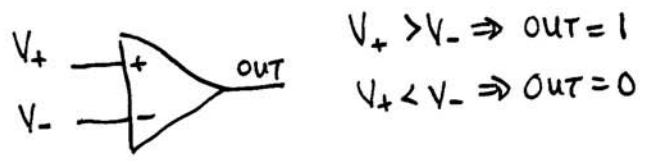There are many types of ADCs. The two we'll discuss both use a comparator:



Successive Approximation ADC

e.g. for 3-bit converter

VIN	D2	D1	D0
-0.5 to 0.5V	0	0	0
0.5V to 1.5V	0	0	1
1.5V to 2.5V	0	1	0
2.5V to 3.5V	0	1	1
3.5V to 4.5V	1	0	0
4.5V to 5.5V	1	0	1
5.5V to 6.5V	1	1	0
6.5V to 7.5V	1	1	1

⇒ Completes conversion in n-cycles  
a good tradeoff between speed, number of bits, & cost

First guess: 3.5V  
if too high ⇒ D2 = 0  
if too low ⇒ D2 = 1  
Say Vin = 2.1V ⇒ too high  
Second guess: 1.5V  
if too high ⇒ D1 = 0  
if too low ⇒ D1 = 1  
Vin = 2.1V ⇒ too low  
Third guess: 2.5V  
if too high ⇒ D0 = 0  
if too low ⇒ D0 = 1  
Vin = 2.1V ⇒ too low  
⇒ final result is 011