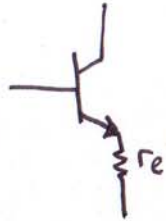


Effective emitter resistance

Ebers-Moll  $\Rightarrow V_{BE} \cong V_T \ln \frac{I_c}{I_s} = V_T [\ln I_c - \ln I_s]$

$\Rightarrow r_e \equiv \frac{dV_{BE}}{dI_c} = \frac{V_T}{I_c}$

$V_T \cong 25 \text{ mV at } RT$




resistance built into the transistor:


$r_e = \frac{25}{I_c} \text{ (} I_c \text{ in mA)}$

Push-Pull Buffer

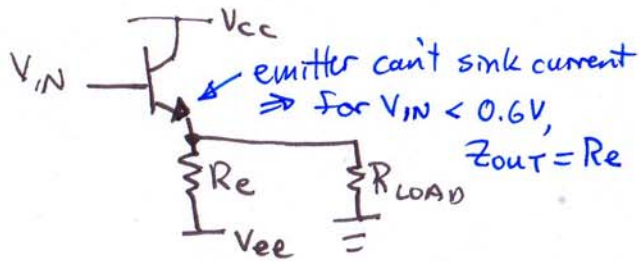NPN-based emitter follower doesn't work well for  $V_{IN} < 0.6V$ :




Solution:

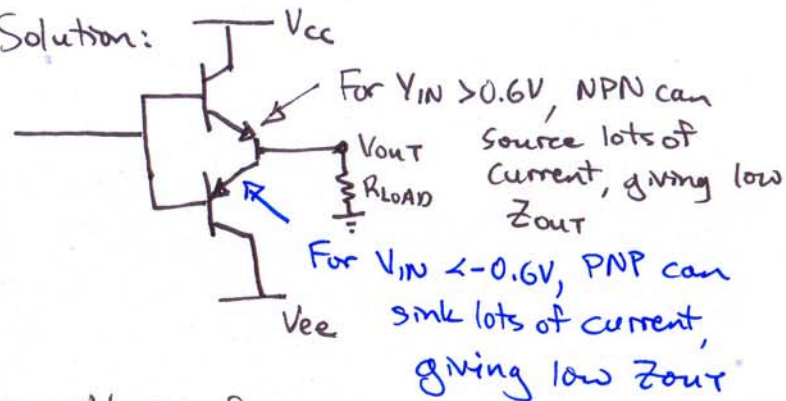

One problem: for  $-0.6 < V_{IN} < 0.6$ , neither ~~the~~ transistor is active  $\Rightarrow V_{OUT} = 0$ . ☹️

Op amps

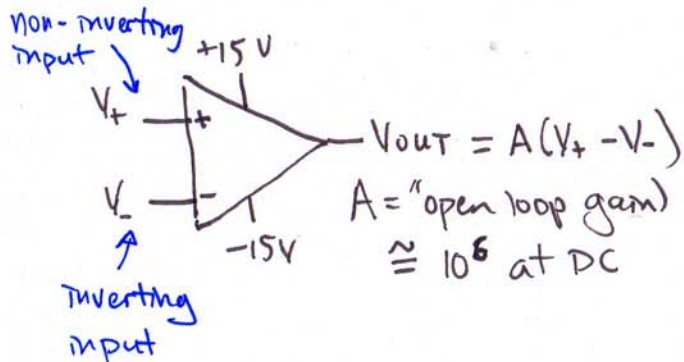

Golden Rules


\* 1) No current flows into inputs \*  
 ( $Z_{in}$  typically  $> 100 M\Omega$  at DC)

$V_{out}$  is between  $\pm 15V$

$\Rightarrow (V_+ - V_-)$  is between  $\pm 15\mu V \approx 0$

$\Rightarrow$  2)  $V_+ \approx V_-$

Example: buffer

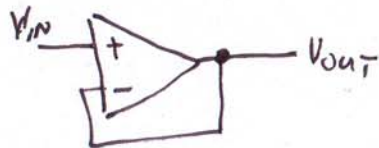

By 2),  $V_- = V_{in}$

because of the wire from  $V_{out}$  to  $V_-$ ,

$V_{out} = V_-$

$\Rightarrow V_{out} = V_{in}$ , as desired for a buffer

Why is  $Z_{out}$  of the buffer so low? feedback!

low  $Z_{out} \Rightarrow V_{out}$  should be constant

If  $V_{out} \downarrow$ ,  $V_- \downarrow$ , then, since  $V_{out} = A(V_+ - V_-)$ , the op amp brings  $V_{out}$  back up!