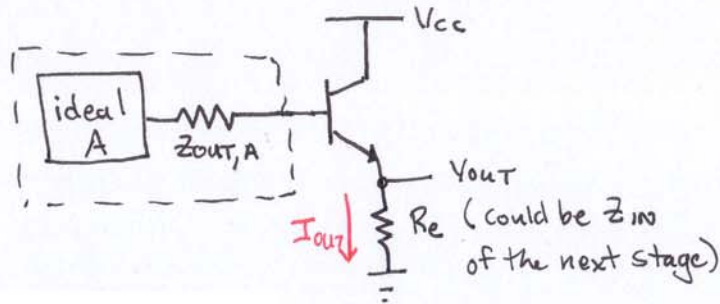


An example of calculating output impedance for circuits including active components (such as transistors): output impedance of an emitter follower



Strategy: "Apply" ΔV_{out} , find resulting ΔI_{out} , use $Z_{out} \equiv -\Delta V_{out} / \Delta I_{out}$

$$V_{be} = 0.6V \Rightarrow \Delta V_b = \Delta V_{out} \Rightarrow \Delta I_b = -\Delta V_{out} / Z_{out,A}$$


$$I_c = \beta I_b \Rightarrow \Delta I_c = \beta \Delta I_b = -\beta \Delta V_{out} / Z_{out,A}$$

$$\Delta I_{out} = \Delta I_e = \Delta I_b + \Delta I_c = -(1+\beta) \Delta V_{out} / Z_{out,A}$$

$$\Rightarrow Z_{out} = -\frac{\Delta V_{out}}{\Delta I_{out}} = \frac{Z_{out,A}}{1+\beta}$$

\Rightarrow output impedance reduced by $(1+\beta) \approx 100$.

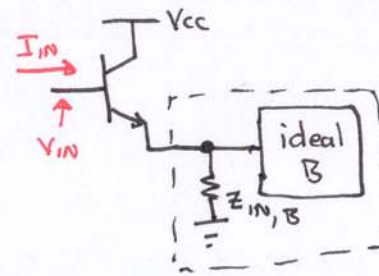An example of calculating input impedance for circuits including active components: input impedance of an emitter follower



Strategy: apply ΔV_{in} , find resulting ΔI_{in} , use $Z_{in} \equiv \Delta V_{in} / \Delta I_{in}$

$$V_{be} = 0.6V \Rightarrow \Delta V_{out} = \Delta V_{in}$$

$$\Rightarrow \Delta I_{out} = \Delta V_{in} / Z_{in,B}$$

$$\text{But we also have } \Delta I_{out} = \Delta I_b + \Delta I_c \left. \begin{array}{l} \Delta I_c = \Delta I_b \cdot \beta \end{array} \right\} \Rightarrow \Delta I_{out} = \Delta I_b (1+\beta)$$

$$\Leftrightarrow \Delta I_b = \frac{\Delta I_{out}}{1+\beta} = \frac{\Delta V_{in}}{Z_{in,B} (1+\beta)}$$


$$\Delta I_{in} = \Delta I_b$$

$$Z_{in} = \frac{\Delta V_{in}}{\Delta I_{in}} = Z_{in,B} (1+\beta)$$


\Rightarrow input impedance increased by $(1+\beta)$!

Ebers-Moll model for transistors

Our simple model:

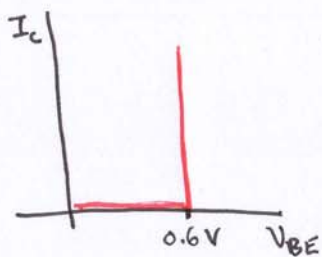

Reality, Ebers-Moll model:

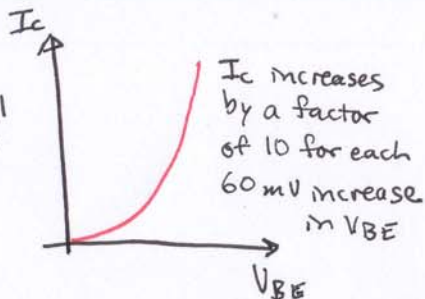

"transconductance" $g_m \equiv \frac{dI_c}{dV_{BE}}$
is large for bipolar transistors

$$I_c = I_s (e^{V_{BE}/V_T} - 1)$$

\uparrow depends strongly on T, transistor type

$$V_T \equiv \frac{kT}{e} = 25.3 \text{ mV at room temp. } \Rightarrow \text{ typically, } e^{V_{BE}/V_T} \gg 1, I_c \approx I_s e^{V_{BE}/V_T}$$

$$\Rightarrow V_{BE} \approx V_T \ln \frac{I_c}{I_s}$$