

Physics 326a-2011 Class 2 Thursday/Friday 9/1-2/11 Summary


Complex version of Ohm's Law

$\tilde{V} = \tilde{I} Z$, where actual $V = \text{Re } \tilde{V}$
actual $I = \text{Re } \tilde{I}$

Impedance of a capacitor

$\tilde{V} = \tilde{I} Z$
 $Q = CV$ } $\rightarrow Z_c = \frac{1}{i\omega C}$ *

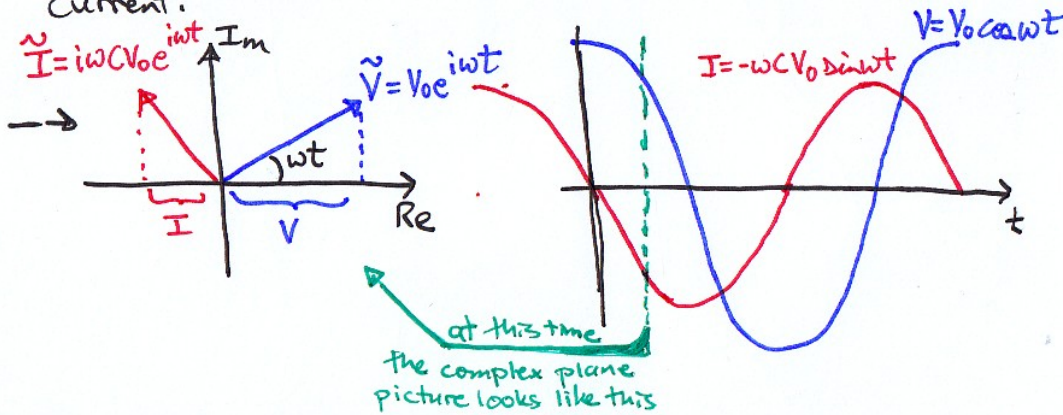Apply $V = V_0 \cos \omega t$ to a capacitor. What is the resulting current?




The current leads the voltage. (Must charge up the capacitor for voltage to appear.)


Phase shift in a low-pass filter

\rightarrow At low freq, $V_{out} = V_{in}$ (no phase shift)
At high freq, phase shift $\rightarrow -90^\circ$.

At medium frequency:

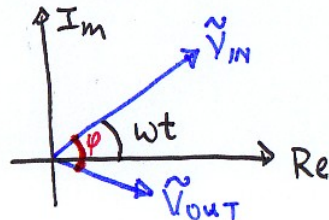

One can show, for low-pass filter:

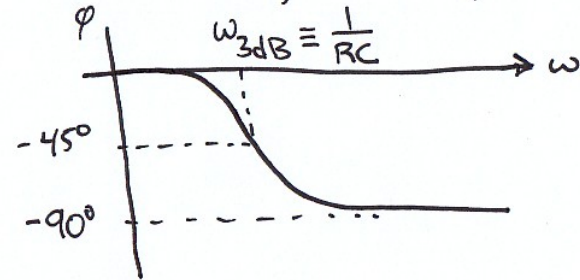

Decibels

$dB = 20 \log_{10} \frac{V}{V_{ref}} \Rightarrow V = V_{ref} 10^{dB/20}$ *

- \rightarrow change of 3dB \leftrightarrow factor of $\sqrt{2}$
- \rightarrow at $\omega = \omega_{3dB}$, $\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}}$ for low pass

Note: $P \propto V^2 \Rightarrow 10dB \leftrightarrow$ factor of $\sqrt{10}$ change in V
factor of 10 change in P

Bandwidth of an amplifier

The frequency at which the gain is reduced by $\sqrt{2}$

Better model for 10X probe

