

### Waves on transmission lines

**Transmission line:** A pair of conductors used to transmit a signal. The current in on one conductor equals the current out on the other.

Even straight wires have associated inductance.

$L_0 \equiv$  inductance per meter


$C_0 \equiv$  Capacitance per meter (between the two conductors)

$\rightarrow$	em waves	isomorphic	waves on transmission lines
*	E	$\leftrightarrow$	V
	B	$\leftrightarrow$	$L_0 I$
	$\epsilon_0$	$\leftrightarrow$	$C_0$
	$\mu_0$	$\leftrightarrow$	$L_0$

$\Rightarrow v_p = \frac{1}{\sqrt{L_0 C_0}}$  (= 28 m/s for standard coax)

$V = \sqrt{\frac{L_0}{C_0}} I \Rightarrow$  current in the top wire is in phase w/ the voltage

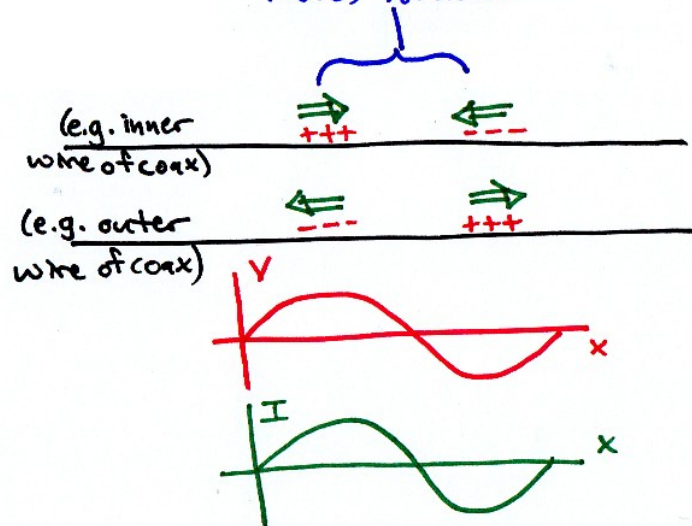You can see how the current flowing in here will charge up the capacitance, so that the voltage peak moves forward



### Left-moving waves on transmission lines

$\rightarrow I$  &  $V$  are 180° out of phase